

11.2


(a)

$R = 1$ and $H = 0$ cannot occur at the same time.

(b)

R	H	Q	Q^+	$Q^+ = R + HQ$
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	X	
1	0	1	X	
1	1	0	1	
1	1	1	1	

(c)

 

11.4 See p. 752 in the textbook

11.6

(a)

S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		S	
R	Q	0	1
0	0	0	1
0	1	1	1
1	1	0	0
1	0	0	0

$Q^+ = R'Q + S R'$

(b) See p. 752 in the textbook

11.9 See p. 753 in the textbook

11.12

For circuit (a) and (b),

When $S = R = 1$, in (a), both outputs are 1, and in (b), the latch holds its state.


When $S = R = 0$, both Q in (a) and (b) will holding it's state.

When $S = 0, R = 1$, both Q in (a) and (b) will be set to 0.

When $S = 1, R = 0$, both Q in (a) and (b) will be set to 1.

S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1

11.24

 

11.26

