
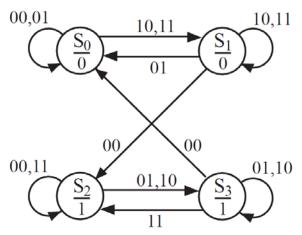
14.4 see p.741 in the textbook14.5 see p.741 in the textbook14.6




State	Meaning	
S_{0}	Z=0 and last input was either 00 or 01	
S_1	Z = 0 and last input was either 10 or 11	
S_2	Z = 1 and last input was either 00 or 11	
S_3	Z = 1 and last input was either 01 or 10	

	Next State	
State	$X_1 X_2 = 00 \ 01 \ 10 \ 11$	Z
S_{0}	S_0 S_0 S_1 S_1	0
$S_{_{1}}$	S_2 S_0 S_1 S_1	0
S_{2}	S_2 S_3 S_3 S_2	1
S_3	S_0 S_3 S_3 S_2	1

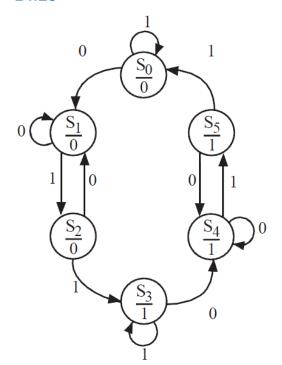14.10 see p.763 in the textbook **14.26**




14.34

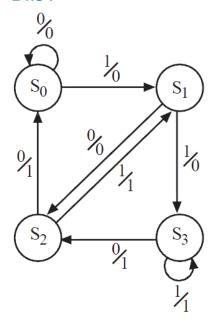

	Next State		,	Z
State	X=0	X=1	X=0	X=1
S_{0}	S_{0}	S_{1}	0	0
S_{1}	S_{2}	$S_{_{3}}$	0	0
S_{2}	S_{0}	S_{1}	1	1
S_3	S_2	S_3	1	1

State	Meaning	
S_{0}	Previous two inputs were 00	
S_{1}	Previous two inputs were 01	
S_2	Previous two inputs were 10	
S_3	Previous two inputs were 11	

14.41

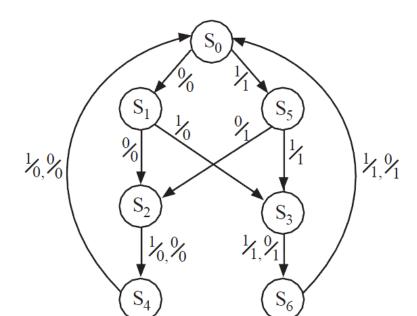

	Next State		Ź	Z
State	X=0	X=1	X=0	X=1
S_0	S_{1}	S_{5}	0	1
S_{1}	S_2	$S_{_{3}}$	0	0
S_2	S_4	S_{4}	0	0
S_3	S_{6}	S_{6}	1	1
S_4	S_{0}	S_{0}	0	0
S_5	S_2	$S_{_{3}}$	1	1
S_6	S_0	S_0	1	1

State	Meaning
S_0	Reset
S_{1}	A = 0
S_5	A = 1
S_{2}, S_{4}	B = 0
S_3, S_6	B=1